



Projects (/circuits/projects/)

Contests (/contest/)

Let's Make...

# Digital Controller for Air Suspension Using Arduino and Smartphone Remote


By XstreamFix (/member/XstreamFix/) in Circuits (/circuits/) > Arduino (/circuits/arduino/projects/) 12,744 23 27 Featured



Download

Favorite

Digital Powered Lift

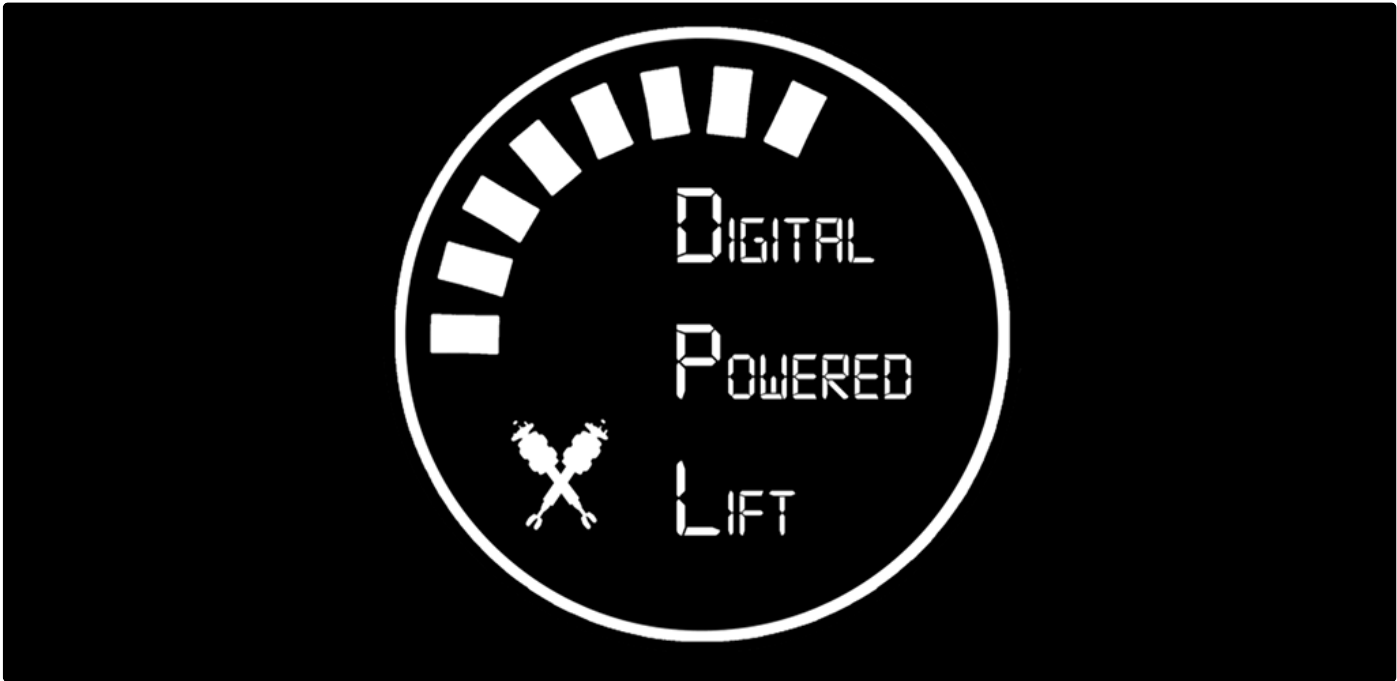



(/member/XstreamFix/)  
By **XstreamFix**  
(/member/XstreamFix/)

Follow

About: From Portugal with Love :D More About XstreamFix »  
(/member/XstreamFix/)

## Hello everyone.

In this instructable i will try to show you how to build a controller for you car air suspension, using one arduino + bluetooth module and for remote any smartphone with android +4.4 , this is also my very first instructable so bear with me please :)

This project began with a friend that had air suspension installed but no digital controller, so on my spare time i decided to see if i could build one for him, later i decided to try and sell the idea but here in Portugal no one seemed interested and since i don't even own a car with air installed, now, i'm going to share the project with everyone.

The hardware and software on arduino is made to work with the DigitalPowerLift apk on a Smartphone, it works on suspensions with 4 solenoids or with 8 also there are 3 buttons on this hardware so that you can adjust the car height without the phone.

My next step with this project was going to be height sensors for each wheel and activate the Auto-Mode within the apk but, again, as i don't even have a car with air to try stuff everyday is there but just showing speed.


This project need's some other components to build because the arduino alone cannot activate the 12v solenoids on the air valves, and some sort of regulator to supply power to the arduino because of the spikes on the car 12v line "just in case", this project can also use the same layout for other projects that require the activation of solenoids via smartphone.

With this instructable you will also learn how to apply voltage dividers to your project, using several pushbuttons with your arduino plugged only to one analog pin, using transistors to activate a bigger load than the arduino 5v.

You will be able to download all the code for the arduino just some steps ahead, for the smartphone the apk DigitalPowerLift can be downloaded from google play.

I will show how to assemble everything onto a breadboard but i have 2 examples "check the last video" of all the components in a small pcb , for those you will need some soldering skills.

 Add Tip

 Ask Question

 Comment

Download

---

## Step 1: Components

---

### **Components list:**

*TIP120 -Transistor ---- 8*

*N4007 -Standard Diode ---- 8*

*Resistor 1K ---- 9*

*Resistor 1K8 ---- 1*

*Resistor 390k ---- 1*

*Resistor 470k ---- 3*

*PushButton ---- 3*

*Led 3mm Green ---- 4*

*Led 3mm Red ---- 4*

*Optional - DC-DC Step Down 4.5V- 60V to 3-35V ---- 1*

*Bluetooth Module HC-05*

*Arduino*


*Breadboard 830 point*

*Breadboard jumpercables*

**Note:** If in your car you only have 2 solenoids for each axle you only need 2 of each Led's, 4 - TIP120 and 4 - Diodes Any of these arduino's will do "Uno, Pro mini, Breaduino" other's will also work but some change's to the voltage of the step-down and in the code pin-out needs to be edited before uploading.



Add Tip

 Ask Question

 Comment

Download

---

## Step 2: Assembly Order

Just the way i think it is easier to connect everything to the breadboard.

### Assembly Order:

1. Start by connecting you arduino to the power rails on the breadboard 5v and Gnd on both sides.
2. Connect the Bluetooth module.
3. Connect all the transistors.
4. Connect all the buttons.
5. **Share the GND connections from the car with the breadboard.**
6. Use the step-down to power the arduino "in case you have it.
7. Upload the code to the arduino.
8. Install the application on your smartphone.

9. Open the Serial monitor, make sure the pushbuttons are working "text will appear on serial monitor" lights should light up as you push them.
10. Identify all the transistor output so you can connect the correct wheel up or down in the car.

[Add Tip](#)[Ask Question](#)[Comment](#)[Download](#)

---

### Step 3: Bluetooth Module & Button's

Assuming that some of you never used a bluetooth module or a transistor i decided to make a small guide about how to connect everything in detail, these are the first. You can follow the images to help you connect everything well.

### **Bluetooth Module:**

First we need to lower the arduino Rx wich is 5v to 3.3v the easiest and cheapest way is making a voltage divider, as you can see in the picture is very simple.

1. Connect the +5v and GND of the module
2. Just connect one end of the 1k8 resistor to ground and the other near the module at the 1st hole of the rail.
3. Connect one end of the 1k resistor in the same rail as of the 1k8 just leave a hole between them, the other end of the 1k resistor connect somewhere else.
4. Connect a cable on digital pin 10 arduino to the RX of the bluetooth module.
5. Connect a cable on digital pin 11 arduino to the rail where the 1k resistor is lonely.

Finally connect a cable to the same rail where the two resistors meet, insert the cable right between them and the other end to the TX module.

### **Pushbuttons:**

Since i was building this project thinking of reading values from analog pins i needed to keep pin's on the arduino free and with 8 solenoids to operate plus the 2 pins from bluetooth module they were going down fast, so i decided to use the 3 buttons on the same arduino analog pin using a connection as you can see in the image.

**Note: For these buttons to work you will need to use the exact same resistor's that i used or you will need to change the code.**

1. Insert the pushbuttons.
2. Connect all of them to +5v on the same first leg.
3. On the other side of the breadboard connect the 470k resistors in series on the opposite leg of the +5v and the last resistor to one empty rail.
4. Now just do the same as the voltage divider with the bluetooth module, connect one end of the 390k resistor to ground and the other to the same rail where the 470k is alone leave a hole between them.
5. Finally connect a cable from in between the resistors to the analog pin A1 on the arduino.



Add Tip



Ask Question



Comment

Download

---

## **Step 4: Transistors**

```
auto=world95fd/moort9shid4thrt49M18hmbi6t41D72AB3F4H6GHH8DIA6F7hKME754H2G7N1B6E73N9882odcf6f2 auto=world95fd/moort9shid4thrt49M18hmbi6t41D72AB3F4H6GHH8DIA6F7hKME754H2G7N1B6E73N9882odcf6f2
```

## Now the transistors

This is simple, just start by connecting one like the image and repeat for the rest of them.

In this step you need to know how the diode works, if you don't is really simple. Just imagine it as a river that only flows one way, since we will be working with GND to activate the solenoid's we must connect the end of the diode that has a little silver ring around it, to the + and the other end on the same rail as the middle pin on the TIP120, this is to prevent frying your transistor because the solenoids are like a DC engine, when you release them they will produce for a short time current that will try to travel back to the transistor so we need to dump it to the + again. "Use the images supplied for help and examples"

If your air ride installation only have 4 solenoids,,pay attention to the last note.

### **Steps:**

1. Facing the text on the transistor the left pin is where you must connect one end of the 1k resistor the other to a empty rail, also connect the Led long leg "Anode" in the same left pin and the short leg "Cathode" to the GND.
2. On the middle pin rail connect the diode near the transistor and one cable lead after the diode "follow the image instructions" , "the cable lead is what is going to connect to the GND of the solenoid".
3. The right pin is shared among all the transistors, this must also be shared with car Ground and Arduino GND.
4. Connect one cable from Arduino digital pin 2 to the alone end of the 1k resistor.
5. Repeat for all the transistors from digital pin 2 until digital pin9, see below some Label to how to connect to you car air system .

### **Arduino - transistor connections:**

#### **Green Leds are for UP:**

Digital pin 2 - Front left wheel Up

Digital pin 3 - Front right wheel Up

Digital pin 4 - Back left wheel Up

Digital pin 5 - Back right wheel Up

#### **Red Leds are for Down:**

Digital pin 6 - Front left wheel Down

Digital pin 7 - Front right wheel Down

Digital pin 8 - Back left wheel Down

Digital pin 9 - Back right wheel Down

### **Note:**

For air ride installation's that instead of independent wheel control "8 solenoids" only have control for each axle "4 solenoids" connect like this.

### **Green Led:**




Digital pin 2 - Front axle Up

Digital pin 4 - Back axle Up

**Red Led:**

Digital pin 6 - Front axle Down

Digital pin 8 - Back axle Down

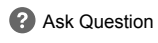

Download

---

## Step 5: Arduino Code

<https://desktop-84m2ab1-8-firebase.firebaseio.com/projects/arduino-code/index.html>

<https://github.com/fitzbr149/fitzbr149.github.io/blob/master/arduino/arduino.ino> <https://github.com/fitzbr149/fitzbr149.github.io/blob/master/arduino/arduino.ino>

If you made all the connections as specified, just upload the code to your arduino.

If not there are some images to help you.

**If you have used different resistors for the buttons you have some help in the images too.**

Download the arduino code here download the code [here](#)

(<https://drive.google.com/file/d/1XAktyaDpg5Hn1Rqm2AQnC-Y8r7p7yZP4/view?usp=sharing>).

**In the images you can find:**

- Where to change baud rates
- Where to change the pins that connect to the transistors and will operate the solenoid's
- Where to change the Bluetooth RX/TX pins
- **If you have used resistors different from instructed in the buttons, some help there.**

If you feel up to it please change the code or use it as you like on your other projects.

"sharing is caring"

**!!Very Important!!**

**Do not change the code where it receives data from the Android Application or else will no work with the android application, only change it if you are sure about what you are doing.**



Add Tip



Ask Question



Comment

Download

## Step 6: Digital Powered Lift App

Digital Powered Lift Instructable



This app is already function with the arduino code.

You can check the video.

To download the application from google play you can find it [here](https://play.google.com/store/apps/details?id=xtreamfix.digitalpowerlift)  
(<https://play.google.com/store/apps/details?id=xtreamfix.digitalpowerlift>).

Just activate your phone Bluetooth, search for and pair your Bt module.

Open the app, go to the top right corner and click for connect, it will then open up a list of paired devices just select the Bt module by clicking it and wait, it should go back with a green ball on top left corner and saying that it is connected.

Everything is working except the Auto-Mode, that currently only displays gps speed.

In the Extra function you position you phone screen facing up and tilt the phone, the car will do the same.

---

## Step 7: Final

How to make Air suspension digital unit for smartpho...



How to make Air suspension digital unit for smartpho...



If you have any doubts or need any help just let me know i will try to help you all the best i can.

You can follow the examples in the video on how to make this in a small pcb very compact and fully working has i have done.

If you are interested that i make a instructable regarding how to make a android application to control arduino projects using android studio let me know in the comment's.

I hope you managed to get this working, and had some fun doing it.

If you also have some tips for fixing or improving my instructable please let me know in the comments also.

Wish you all the best!

:)



Add Tip



Ask Question



Comment

Download

Participated in the  
[Arduino Contest 2017 \(/contest/arduino2017/\)](/contest/arduino2017/)

View Contest

Participated in the  
[Remote Control Contest 2017 \(/contest/rc2017/\)](/contest/rc2017/)

[View Contest](#)

## Be the First to Share

Did you make this project? Share it with us!

[I Made It!](#)

## Recommendations

--	--

(/DIY-REFLOW-OVEN/)

**DIY REFLOW OVEN (/DIY-REFLOW-OVEN/)** by Vulcaman (/member/Vulcaman/) in Electronics (/circuits/electronics/projects/)


♥ 179 👁 9.1K


(/3D-Printed-Mini-CNC-Machine/)


**3D Printed Mini CNC Machine (/3D-Printed-Mini-CNC-Machine/)** by SmartTronix (/member/SmartTronix/) in Arduino


♥ 114 👁 12K

(/contest/trashtreasure2021/) (/contest/microcontroller2021/)



 Add Tip

 Ask Question

 Post Comment

We have a **be nice** policy.  
Please be positive and constructive.

Add Images

Post

## 27 Comments

(/member/dolbtg/) dolbtg (/member/dolbtg/) Question 23 days ago

Answer

▲ Upvote

Hi. I try to build this project ,but i can't find TIP120 in my country. I use TIP122.  
Everything is connected and work. Successful send and recivier data from Android (see in serial monitor). But i have a question - do i have to change the code because i use the different transistors ?  
:)  
volume\_up

(/member/Eyeamfresh1/) Eyeamfresh1 (/member/Eyeamfresh1/) 4 weeks ago

Reply

▲ Upvote

Okay so I am going to be "that guy" but would it be possible to build this on control it off a connected touchscreen?

(/member/Eyeamfresh1/) Eyeamfresh1 (/member/Eyeamfresh1/) Question 4 weeks ago

Answer

▲ Upvote

Any chance you could send me a view from above the headboard or a diagram? I want to build this ASAP for my Audi wagon but have no experience in breadboards. I also want to turn it into a pcb after successfully building it. It would be amazing if you 😊

eyeamfresh@gmail.com (mailto:eyeamfresh@gmail.com)

---

(/member/all4autoeu/) all4autoeu (/member/all4autoeu/) Question 6 weeks ago

Answer

▲ Upvote

i need some help :) i can't find DigitalPowerLift apk in google play..

1 answer ▼

---

(/member/thom+mk4/) thom mk4 (/member/thom+mk4/) 5 months ago

Reply

▲ Upvote

i need some help

i connected everything as in your pics and used everything you did but i keep getting trouble with de led's not turning on

and when i look at the monitor it keeps repeating: change mode

and when it does work it stil doesn't turn on the led's

---

(/member/mbbelgium/) mbbelgium (/member/mbbelgium/) 1 year ago

Reply

▲ Upvote

Hi, Nice project! I think I'm going to duplicate this and I will try to add the pression readings, presets and eventually a small screen with buttons. But glad I found something to start with!

---

(/member/TimD39/) TimD39 (/member/TimD39/) Question 1 year ago

Answer

▲ Upvote

Does your design make automatic height adjustments? I have a Lincoln Navigator with air ride, and I live in Wisconsin. Even if I have no leaks, I know I can have quite the change in air volume/pressure, just from the temperature changes in the day.

If it does adjust automatically, does it have any means of preventing adjustments from happening in the middle of a turn? I know the factory controller in my SUV would prevent that by monitoring the steering wheel.

---

(/member/kauany sophia2018/) kauany sophia2018 (/member/kauany sophia2018/) 1 year ago

Reply

▲ Upvote

amigo posso usa arduino mega

---

(/member/Goldsswagon/) Goldsswagon (/member/Goldsswagon/) Question 1 year ago

Answer

▲ Upvote

You posted using one arduino + bluetooth module and for remote any smartphone with android +4.4. My tablet is 4.4.2 and I get a parsing error. The download app shows android 5.0 and up Version 1.2.

1 answer ▼

---

(/member/DaleC21/) DaleC21 (/member/DaleC21/) Question 1 year ago

Answer

▲ Upvote



Hi. Great tutorial. Have you thought about what it might need to read position levers attached to the axles? So you can have say 3 set positions and the arduino will always maintain that height even if loaded? Love to ahve that function :)

4 answers ▾

(/member/PetrK66/) PetrK66 (/member/PetrK66/) 2 years ago

Reply

▲ Upvote

Hi, I never had a reason to work with Andruino in the past. But as I build my Pontiac Catalina 1965 and have an air chassis, that's exactly what I'm looking for. Perhaps I would like to go to the 8 analog buttons :D and to modify the design of the application but I will start with the first step: D Thx a lot

(/member/RicoD13/) RicoD13 (/member/RicoD13/) 2 years ago

Reply

▲ Upvote

looks really nice i wil build it in a couple of weeks, when i got the parts and air ride.  
Did you write the android app you self?

МартинМ6

(/member/%25D0%259C%25D0%25B0%25D1%2580%25D1%2582%25D0%25B8%25D0%25BD%25D0%259C6/) (/member/%25D0%259C%25D0%25B0%25D1%2580%25D1%2582%25D0%25B8%25D0%25BD%25D0%259C6/) 2 years ago

Reply

▲ Upvote

it's not working... the push buttons work ok, but the android app sends so different numbers then the ones in the sketch and can't control it 2-3 leds tun on and stay on untill you reset it...

1 reply ▾


More Comments


Post Comment

## Categories


 Circuits  
(/circuits/)


 Living  
(/living/)

 Workshop  
(/workshop/)

 Outside  
(/outside/)

 Craft  
(/craft/)

 Teachers  
(/teachers/)

 Cooking  
(/cooking/)

Find Us

## About Us

Who We Are  
(/about/)

Why Publish?  
(/create/)

Jobs (/jobs/)

## Resources

Sitemap (/sitemap/)

Help (/how-to-write-a-great-instructable/)

Contact (/contact/)

(<https://www.instagram.com/instructables/>) (<https://www.pinterest.com/instructables>) (<https://www.facebook.com/instructables>) (<https://www.twitter.com/instructables>)